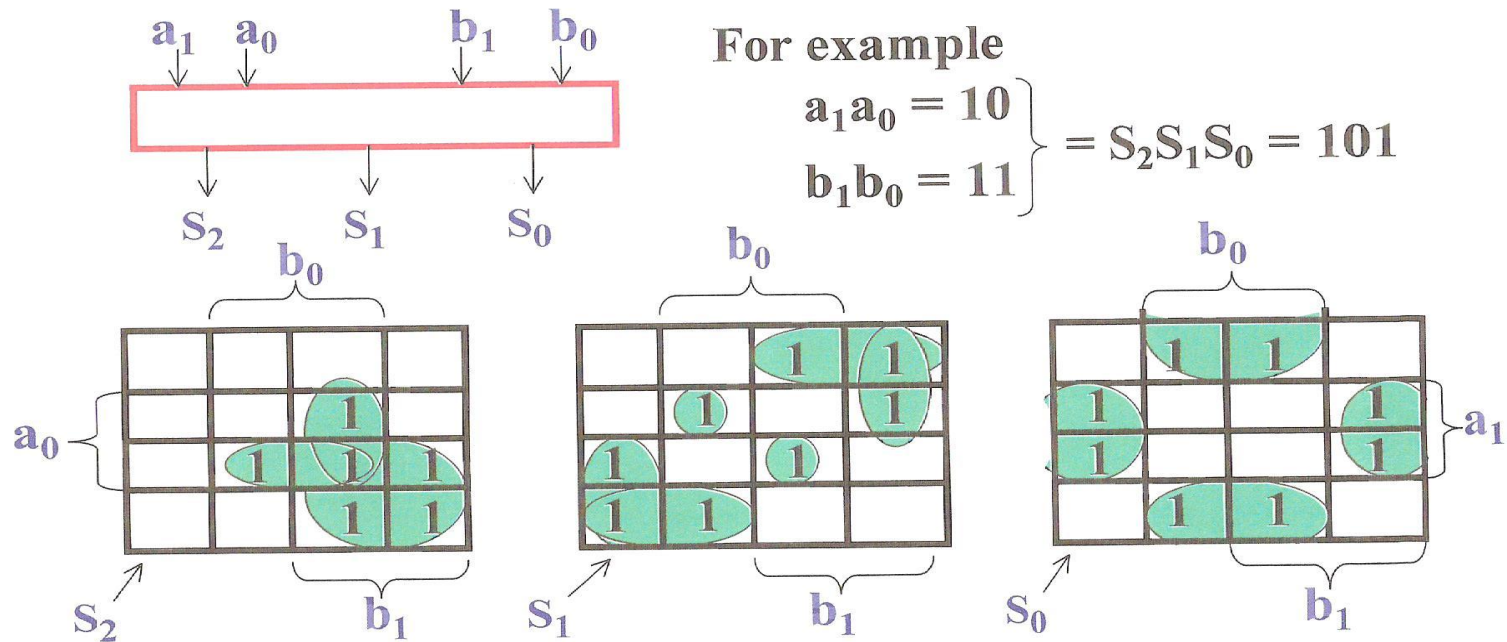


# Three Logical Operations


## Function 4

- 2-bit Parallel Adder (hard)



# Three Logical Operations


## Function 4

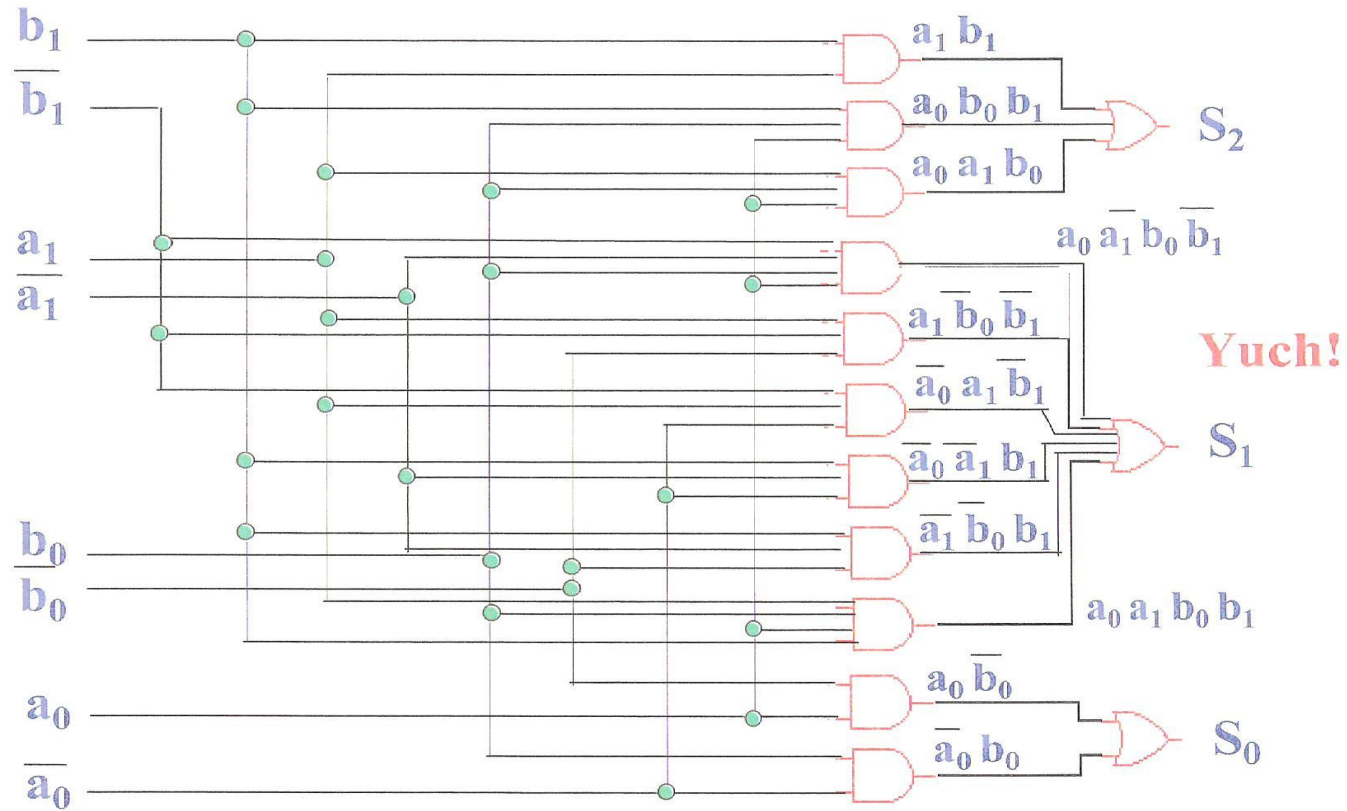

# Three Logical Operations


## Function 4

- Now return to

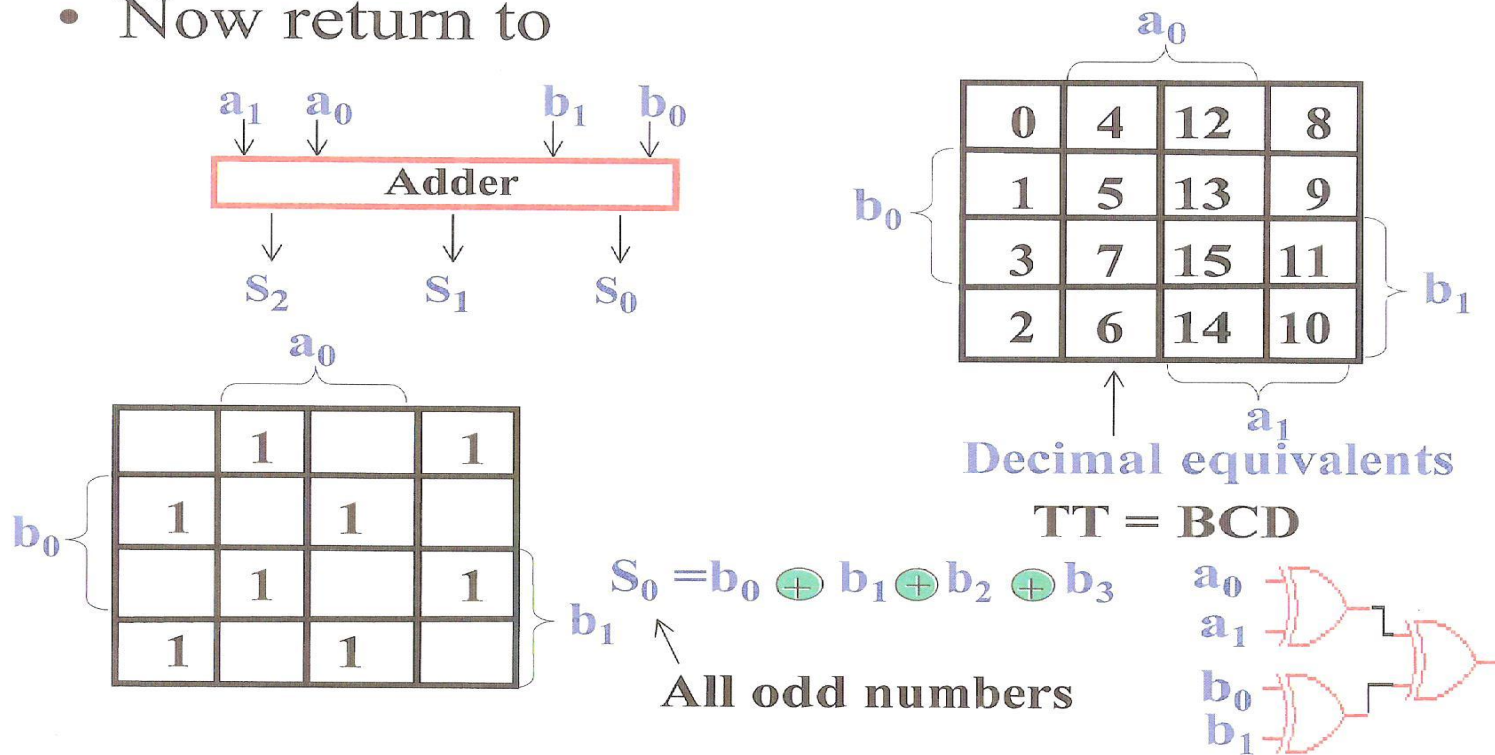

# Three Logical Operations


## Function 4

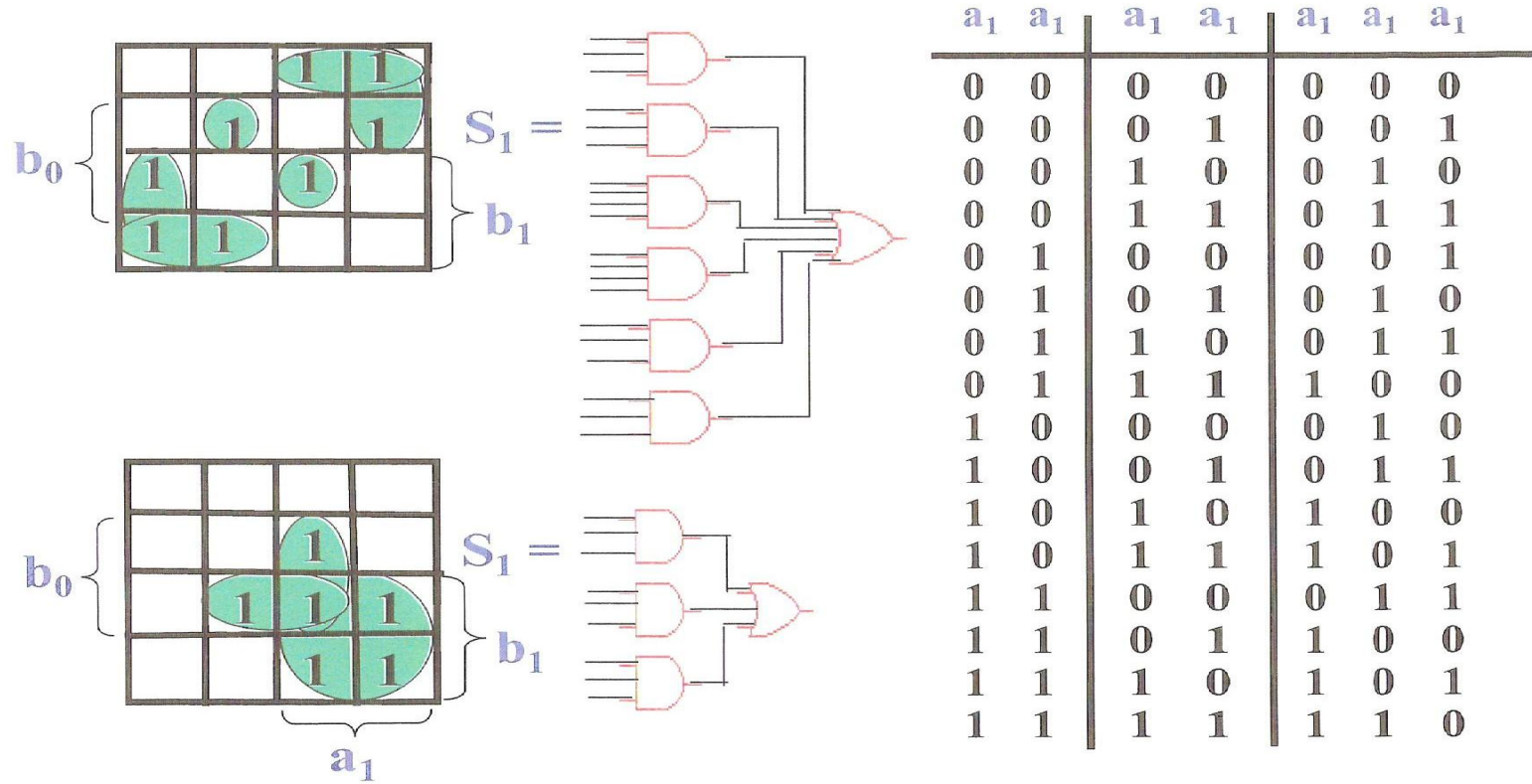

# Three Logical Operations


## Function 4

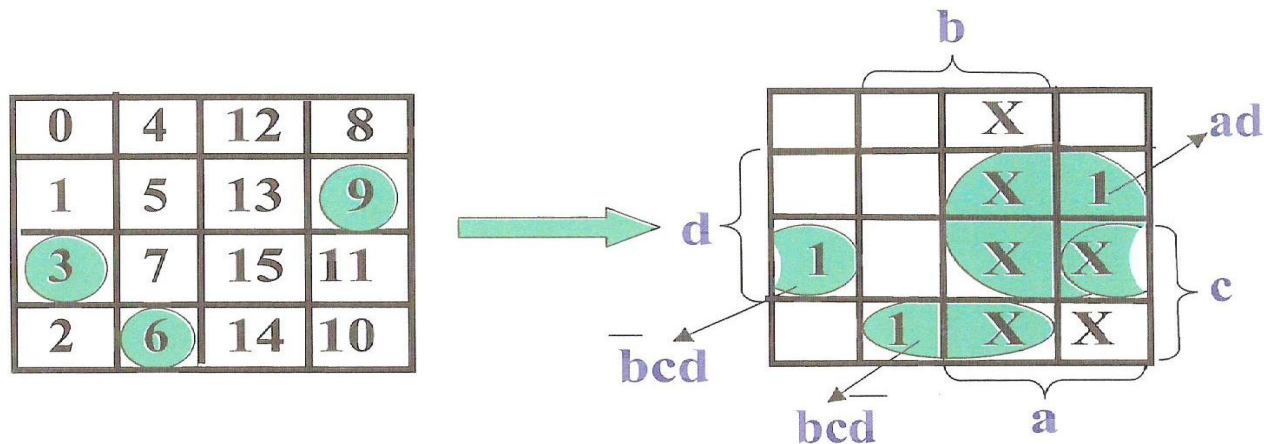- Example Problem: with “Don’t Cares”
  - Which BCD (Binary Coded Decimal) integers are divisible by 3?
  - BCD means 4-bit code but 10-15 not allowed




# Three Logical Operations

## Function 4

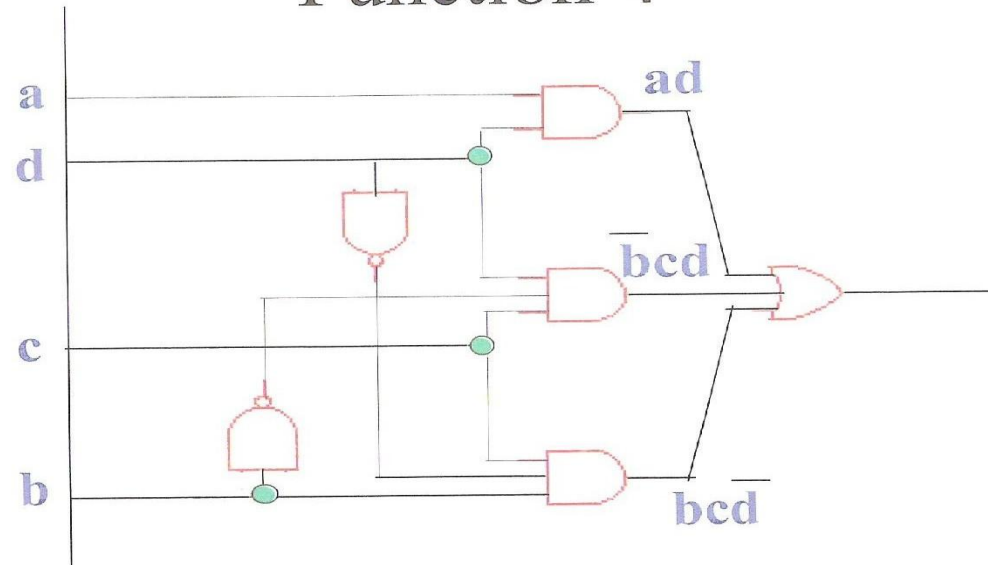

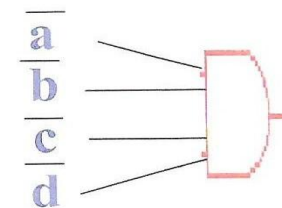
- Is 0 divisible by 3?
  - If so, need another AND gate:



# Three Logical Operations


## Function 4

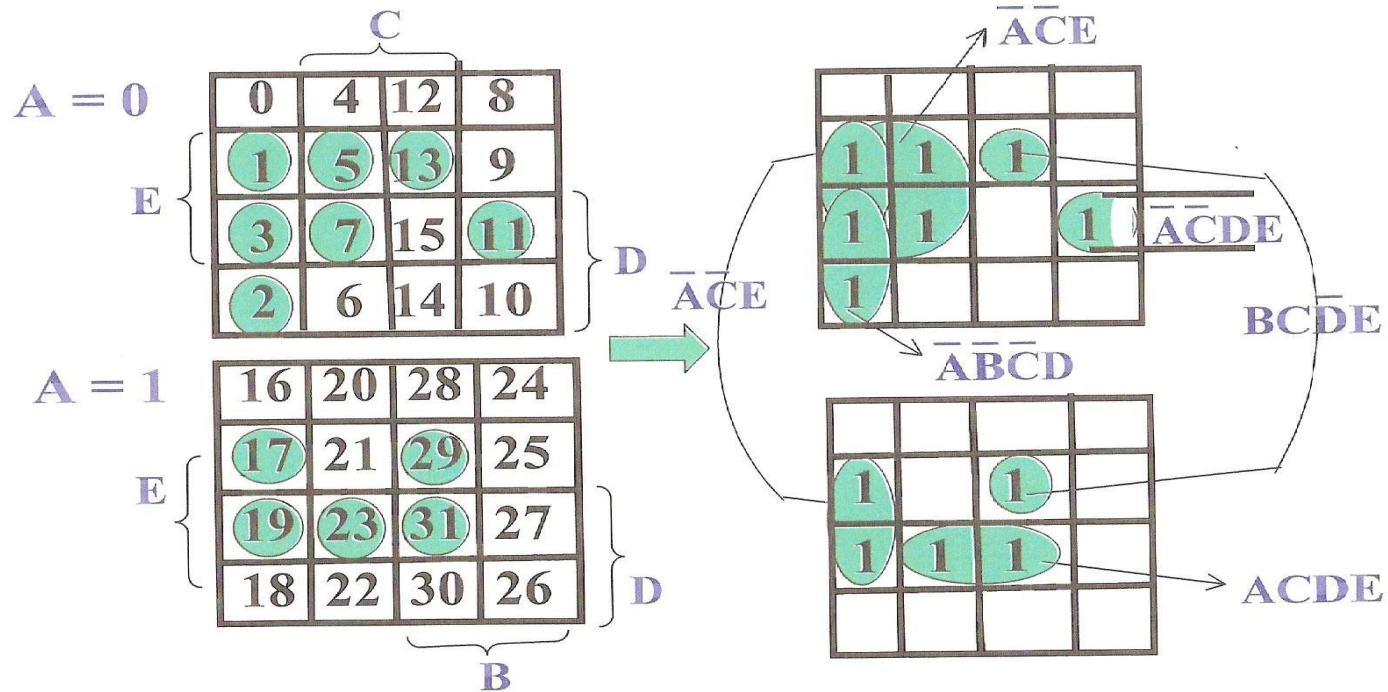- Example Problem: (Very hard)
  - 5 bit Prime Number detector



# Three Logical Operations

## Function 4

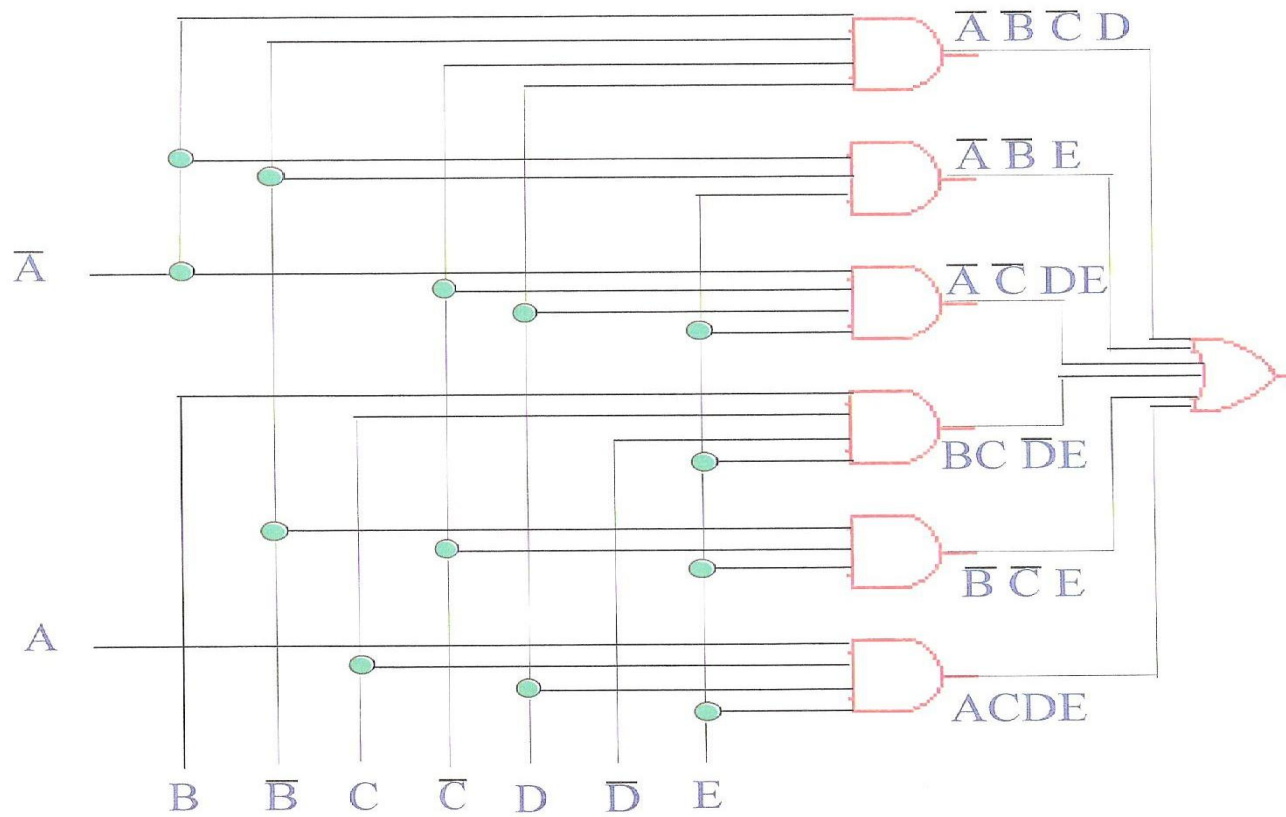


P98-122



# Switches and Relays

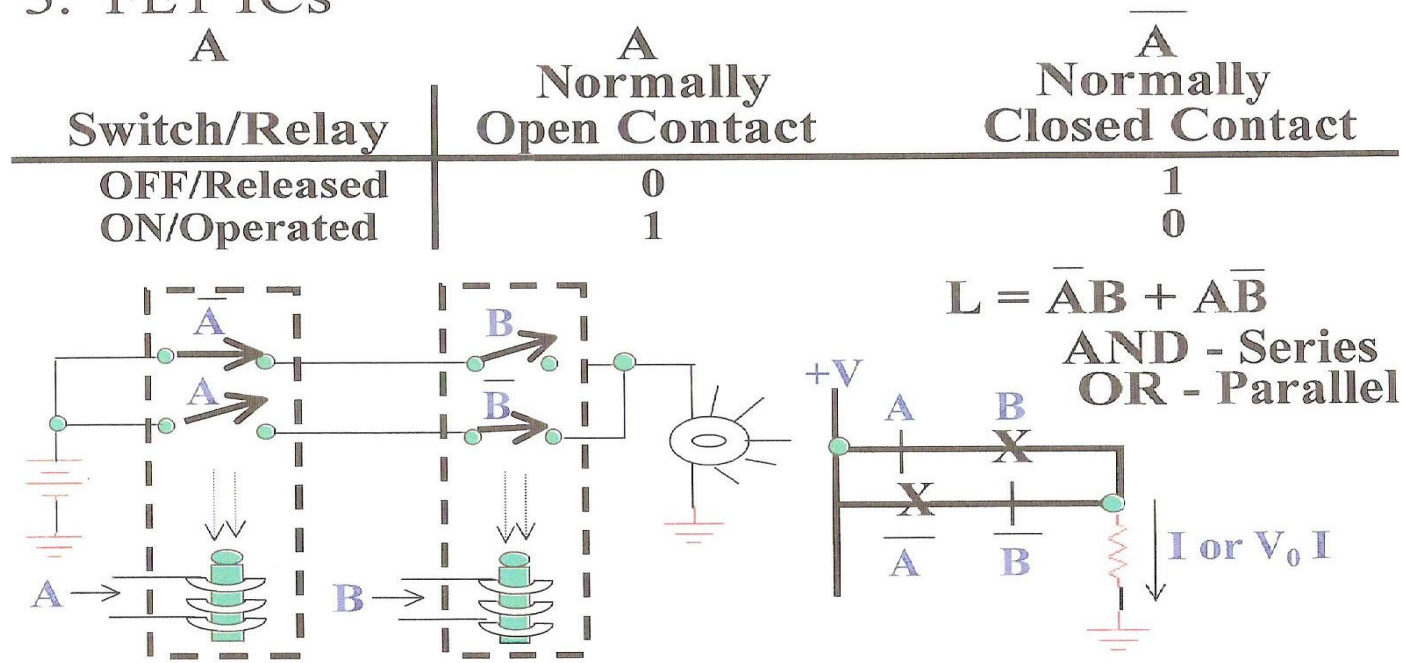- 1. Switches & Relays
- 2. Bipolar Transistor Logic
- 3. FET ICs



# Switches and Relays

- “Transfer Contact”

