

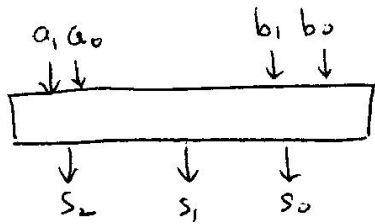



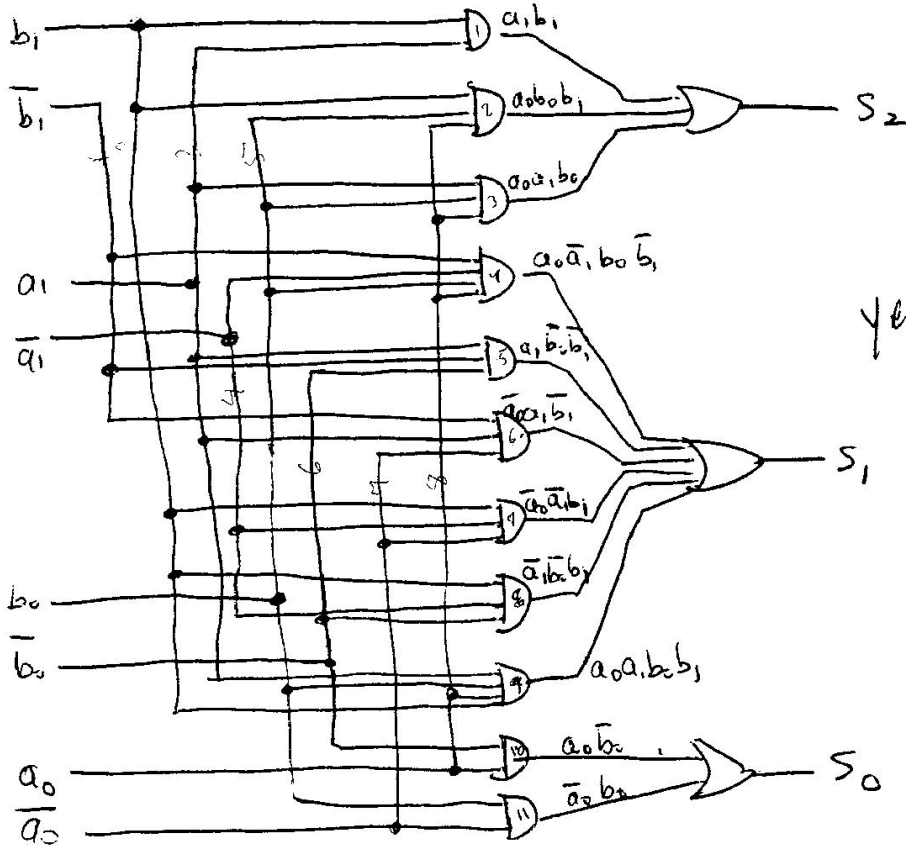
Example Problem 2-bit parallel adder (hard)



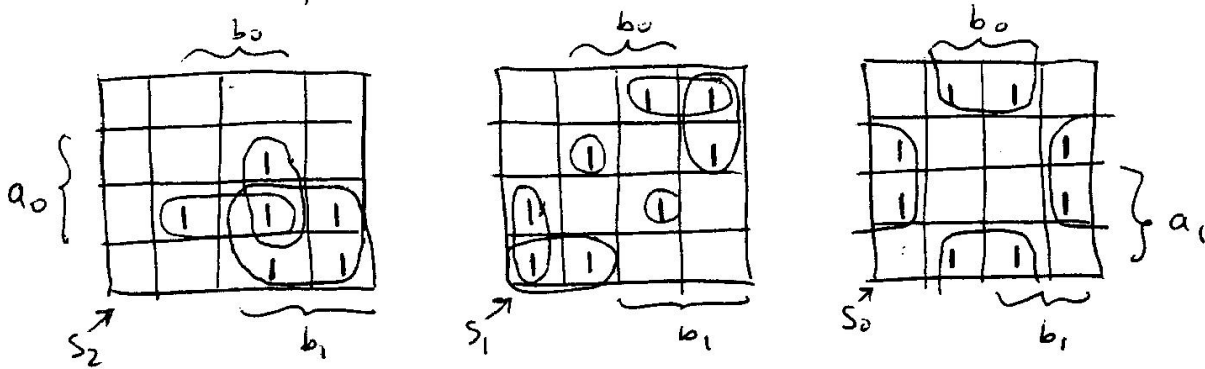for example
 $a_1 a_0 = 10$
 $b_1 b_0 = 11$ } = $s_2 s_1 s_0 = 101$




yeck!

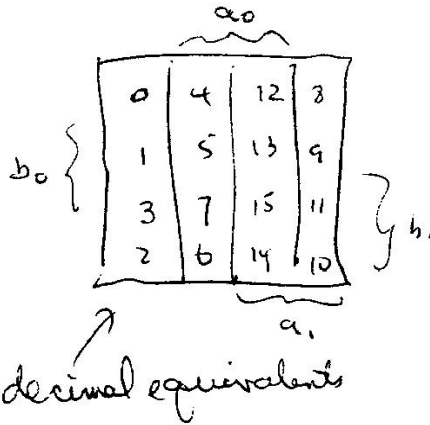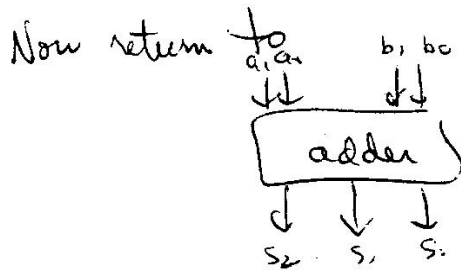





$TT = BCD$

$S_0 = b_0 \oplus b_1 \oplus b_2 \oplus b_3$

all odd numbers


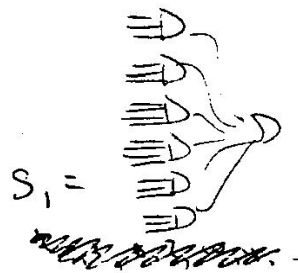


$a_1 a_0$	$b_1 b_0$	$s_2 s_1$
0 0	0 0	0 0
0 0	0 1	0 0
0 0	1 0	0 0
0 0	1 1	0 0
0 1	0 0	0 1
0 1	0 1	0 1
0 1	1 0	0 1
0 1	1 1	1 0
1 0	0 0	0 1
1 0	0 1	0 1
1 0	1 0	1 0
1 0	1 1	1 0
1 1	0 0	0 1
1 1	0 1	1 0
1 1	1 0	1 0
1 1	1 1	1 1

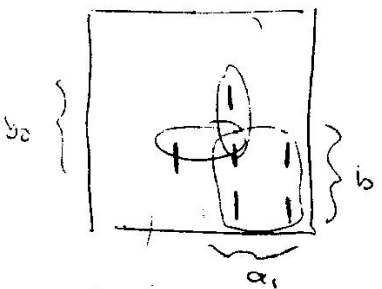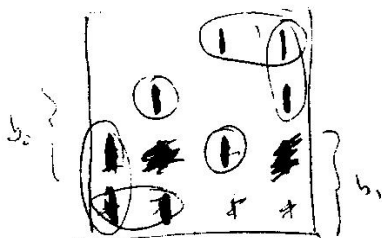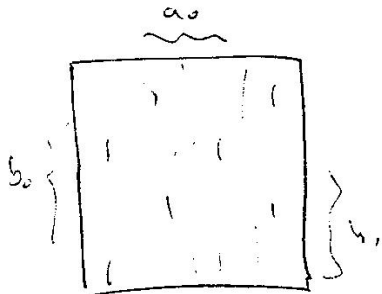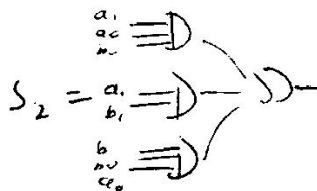

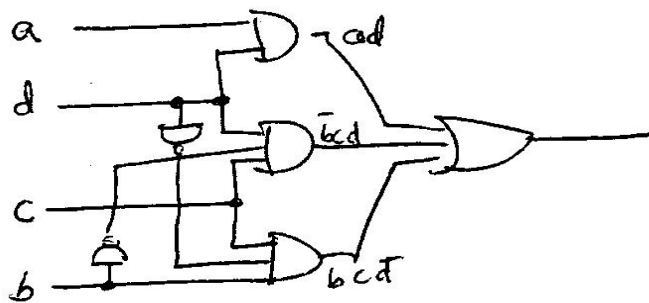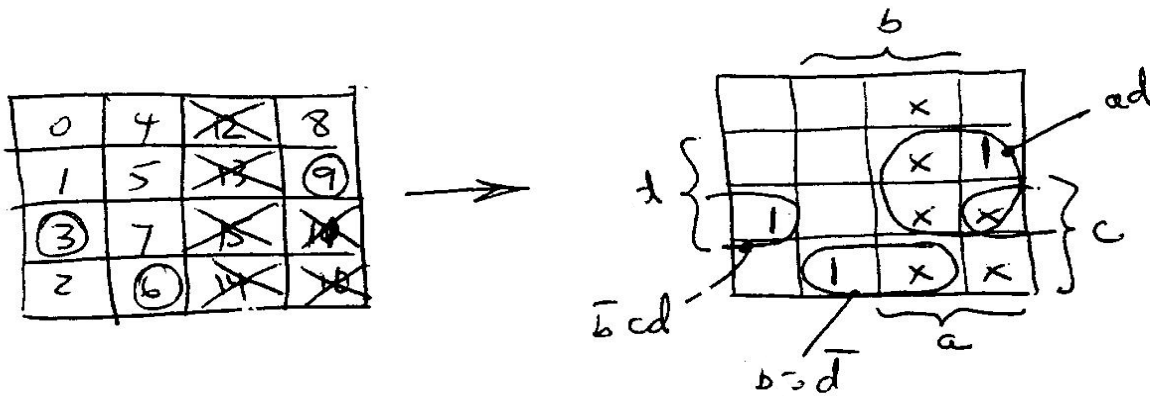
Example Problem with "don't cares"

Which BCD (binary coded decimal) integers are divisible by 3?
 BCD means 4-bit code but 10-15 not allowed



is 0 divisible by 3?

if so, need another AND gate:

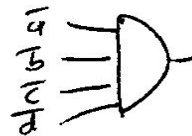

100

Example problem (very hard)

5-bit prime number detector

A=0



	C			
	0	4	12	8
E	①	⑤	⑬	9
	③	⑦	15	⑩
	②	6	14	10

D

A=1

	16	20	28	24
E	⑰	21	⑲	25
	⑱	⑳	31	27
	18	22	30	26

B

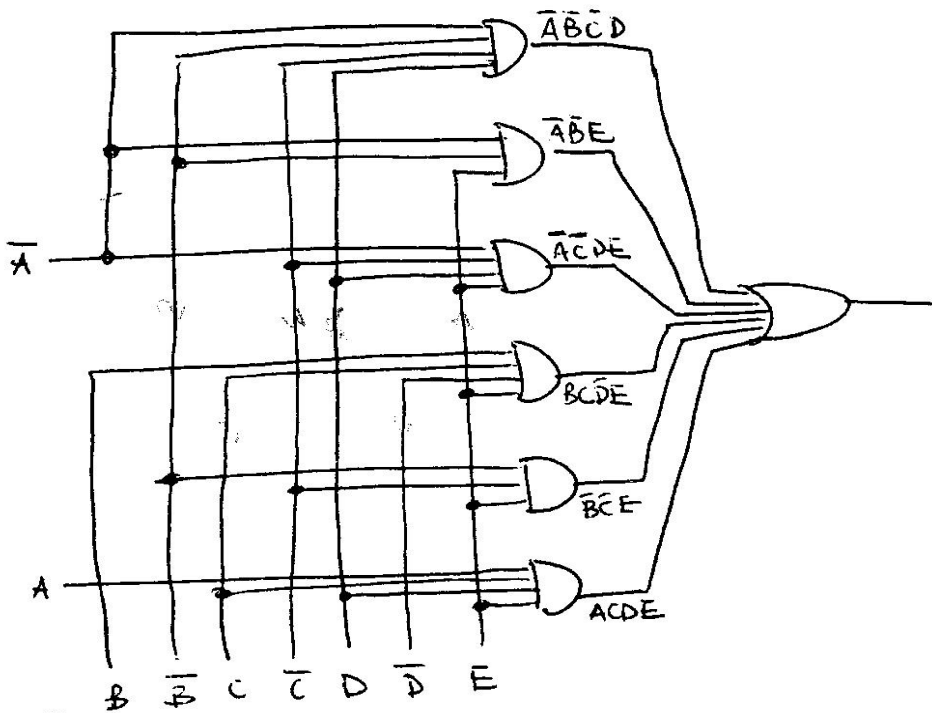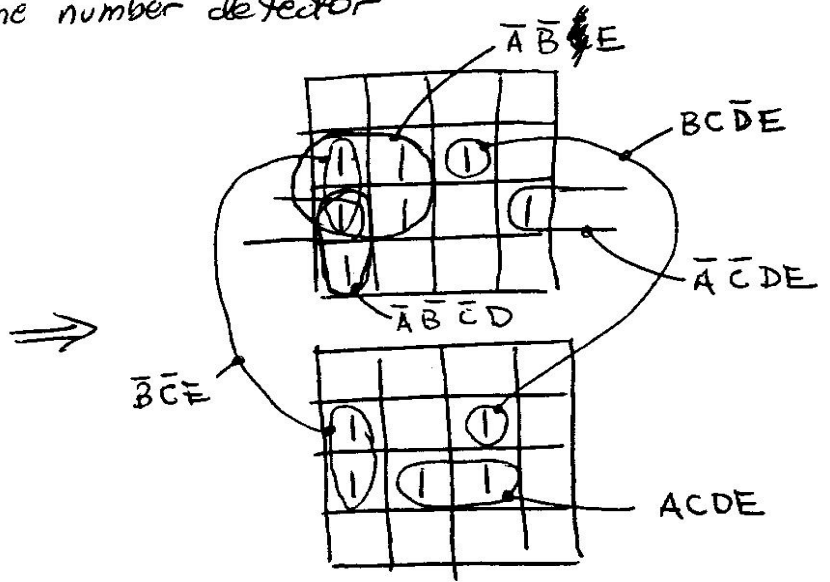

lol


Digital Integrated Circuits

Small Scale Integration


Classical 7400 series TTL

14-pin DIPs


7400 Quad 2-input Nand

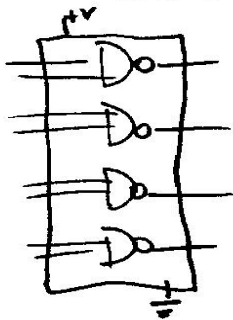


7404 Hex inverter

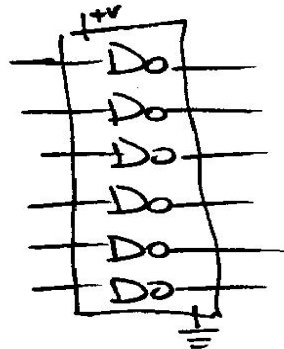

7410 Triple 3-input Nand

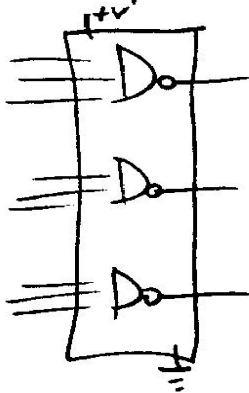

7420 Dual 4 (5) input Nand

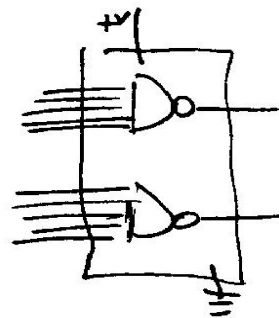

If all chips cost the same: \$C

1 2-input Nand costs \$.25 C

1 4 input Nand costs \$.5 C

can measure effects of gate minimization